

[Products related](#) to this project are for sale. The mosfet amplifier is available as a [complete kit \(PCB + components\)](#) or [PCB-only](#), so you can buy the components yourself. Also the [2SK1058](#) and [2SJ162](#) Mosfets can be ordered separately.

## Introduction

Some time ago, I ordered a book at Amazon named High Power Audio Amplifier Construction Manual by Randy Slone. This book is very much recommended for any one who wants to design an audio amplifier. After reading this book, I decided to try and design a mosfet power amplifier myself, you can read about the result below. I am very pleased with the result, which is really a high-end power amplifier. Not only it looks pretty cool, but also the measurements and listening tests show that this is a top class amplifier, for which I believe there is little room for improvements.


## Specifications

- Max output power: 100W@8ohm, 150W@4ohm
- THD+N (1kHz): < 0.003%
- Noise level: < -100 dB
- Input sensitivity: 1.2V rms
- Input impedance: 22kohm
- Bandwidth: 100kHz
- Voltage gain: 27dB
- Slew rate: 15V/us
- PCB dimensions: 100x60mm
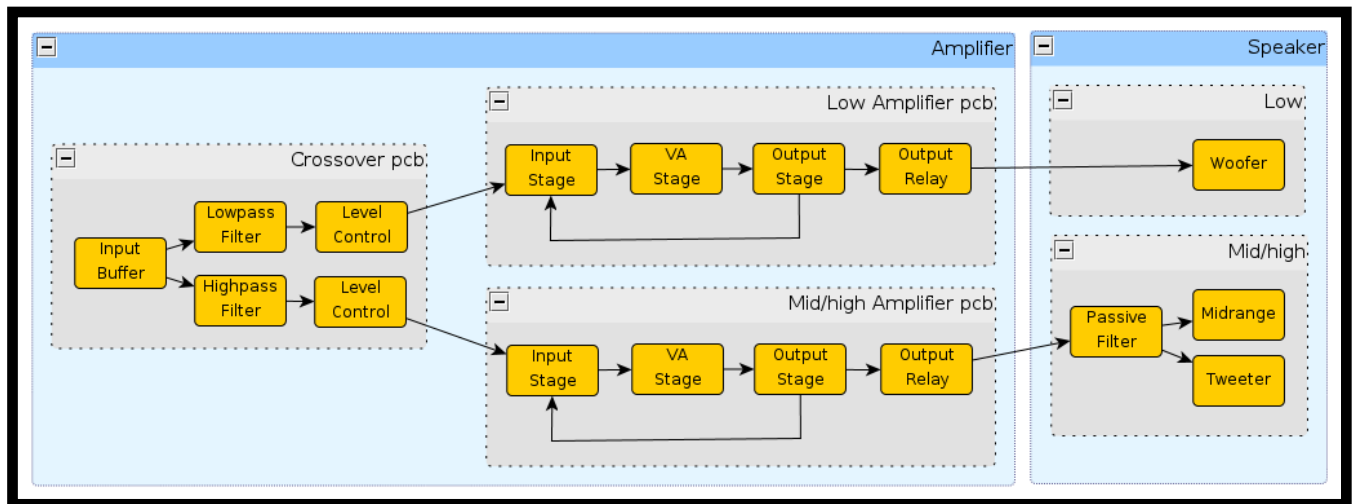
## Design


The main idea behind the design is to build a bi-amping amplifier with separate amplifier boards for the low and mid/high section of each channel, but of course you can also build a normal version by only using one amplifier pcb per channel. The line input signal goes to an active Linkwitz-Riley crossover (-24 dB/decade rolloff) with a crossover frequency at 330 Hz. Both

outputs of the crossover pcb are amplified with identical amplifier pcb's. Four of them are needed for a stereo amplifier. The output of the low frequency amplifier goes to the woofer of a 3-way speaker. The output of the mid/high frequency amplifier goes to the midrange/tweeter of the speaker.


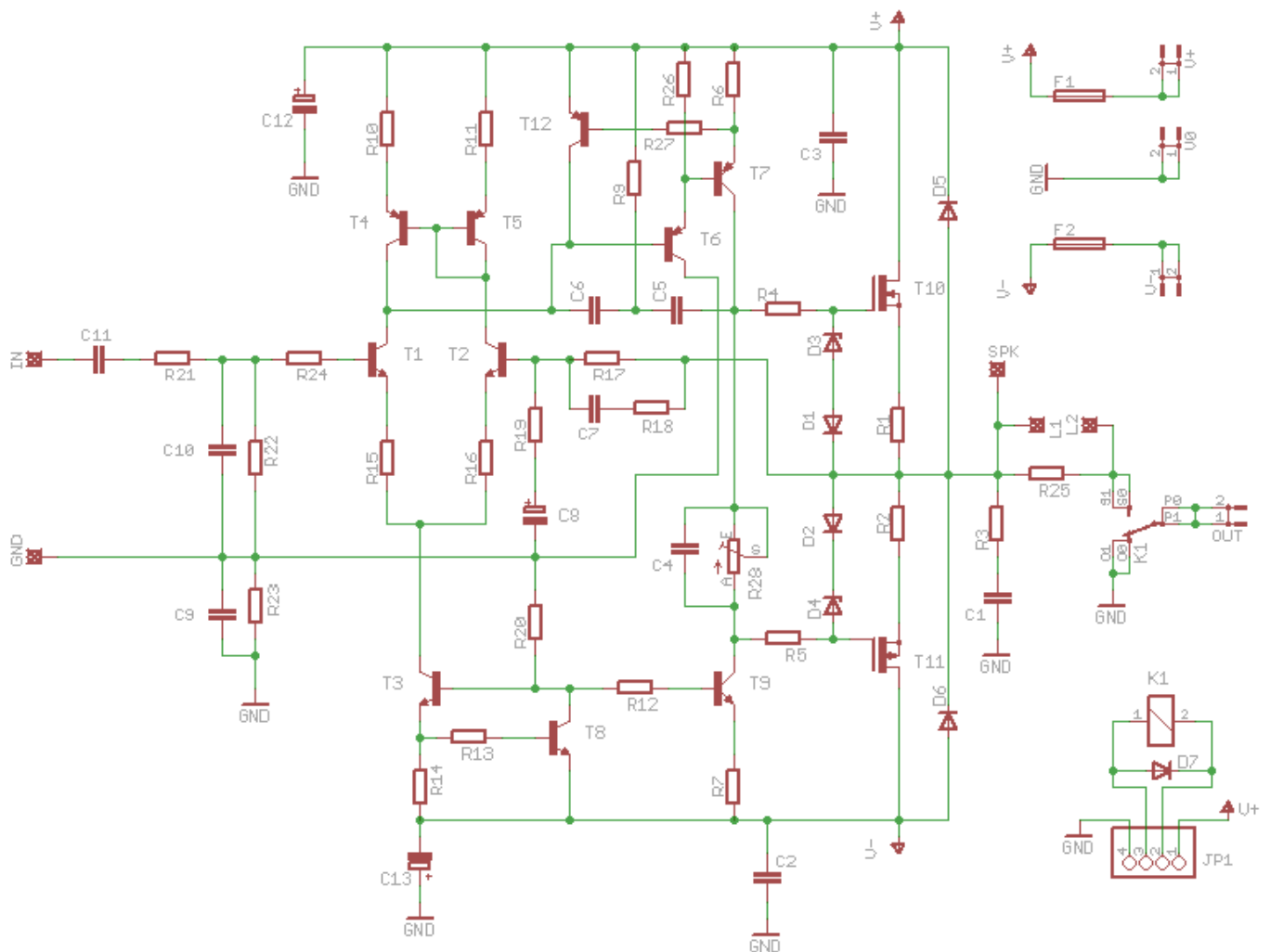
## Amplifier schematic

The amplifier is a quite conventional 3-stage design, with input stage, voltage amplifier stage and output stage, which uses a pair of Hitachi lateral MOSFET's (2SJ162/2SK1058). Apart from the MOSFET's only common and easily available components are used. Component values are not shown, but you can buy the [PCB](#) or a complete [kit](#) in the shop.



The input signal enters the amp through C11 to remove DC (crossover at 7Hz) and is then lowpass filtered (crossover at 130kHz) to prevent high frequency radio signals from entering. The input impedance of 22k is mainly determined by R22. Components around T3 form a current source that feeds the long tailed pair (T1+T2). A current mirror consisting of T4+T5 takes care of balancing the current through the two legs of the LTP. Various emitter degeneration resistors are used to apply local feedback to the transistors and makes operation less sensitive to all kind of variations (temperature, transistor parameters, etc)

This amplifier uses two pole compensation (C5, C6, R9) and an extra driving transistor (T6) to achieve very low distortion levels in the VA stage. The VA stage itself uses a current source (components around T9) and the voltage on the gates of the MOSFETS is controlled by T7. Using R8 the quiescent current through the MOSFETS can be set to decrease crossover distortion. Short circuit protection has been incorporated in the VA stage (R27+T12), which limits the max current through the VA stage to some 20mA. This way, the protection will only have effect when the load connected is less than about 2 ohm (and a large input signal is present).

The Mosfets in the output stage are equipped with zener diodes for basic protection. The global feedback loop is closed by connecting the output through R17 and R19 to the base of T2. AC gain of the amplifier is only determined by the values of R17 and R19 (set to a common 27dB). DC gain is '1' because of C8. The output is connected to the speakers through a damped inductor (L+R25) and output relay. Zobel network (C1+R3) and damped inductor give improved

stability for difficult loads.

## Supply considerations


A schematic of the proposed supply for this amplifier is shown in the following picture. Mains voltage is connected to the primary winding of a preferably toroidal transformer with center-tapped secondary winding. Fuse F1 needs to be chosen in line with your transformer rating. Capacitor C1 prevents high frequency noise from entering/leaving the amp through the supply. Rectification is done with bridge rectifier B1 (or use 4 high power fast recovery diodes). Snubbing capacitors C2-C5 short high frequency switching of the diodes and result in a much cleaner supply. The output of the rectifier is filtered using reservoir capacitors C6-C9. Cheaper and better is to use more low-valued capacitors in parallel, as an example I use 12 times a 2200uF electrolytic capacitor giving 13.200uF per rail. Bleeder resistors R2 and R3 will make sure that the capacitors are safely discharged when you turn off the amplifier.

Always make sure the rail voltage to the amplifiers is taken directly from the capacitors, not from the rectifier. Make a star ground connection (HQGND) by using separate wires to all ground connections in the amplifier including the speaker connections, which is even more important when constructing a stereo amplifier. The mains Earth connection must be connected directly to the chassis of the amplifier. The connection from chassis to the star ground connection using R1 will prevent ground loops and C10 will short high frequency noise.

The bottom part of the figure is only needed if you also need a dual 15V opamp supply, e.g. for a LR filter or integrated preamp. The opamp supply is constructed from the rail voltage in 2 steps: first there is a stepdown converter, which reduces the input voltage for the voltage regulators. The stepdown converter for the positive side consists of R4, D2, C21, which gives a constant 20V at the base of Q2. At the emitter of Q2 this gives approximately 19.3V, which is a nice input voltage for the 7815. The capacitors around IC2 are quite standard, with C16 for instability prevention under varying loads. The negative side works in a similar but mirrored way. This circuit can deliver a maximum of about 150mA, where main power dissipation is done in IC1 and IC2. The power dissipation in IC2 equals  $(V_+ - 19.3) \cdot I_{Q2}$  so with a 48V supply and 150mA this is 4.3W, which can only be achieved with a proper heatsink.

To make the construction of the power supply easier, I designed 2 supply pcb's: a [supply pcb](#) with room for 16 electrolytic capacitors of 18mm diameter and a [supply pcb with integrated 15V dual supply](#) with room for 12 electrolytic capacitors of 18mm diameter. The 2200uF/63V 105deg capacitors I use fit on this pcb giving 2x13.200 uF and 2x17.600 uF respectively. If you think that is not enough, you can even use two (or more) of them, but measurements below show that already excellent results are achieved with 2x13.200 uF!



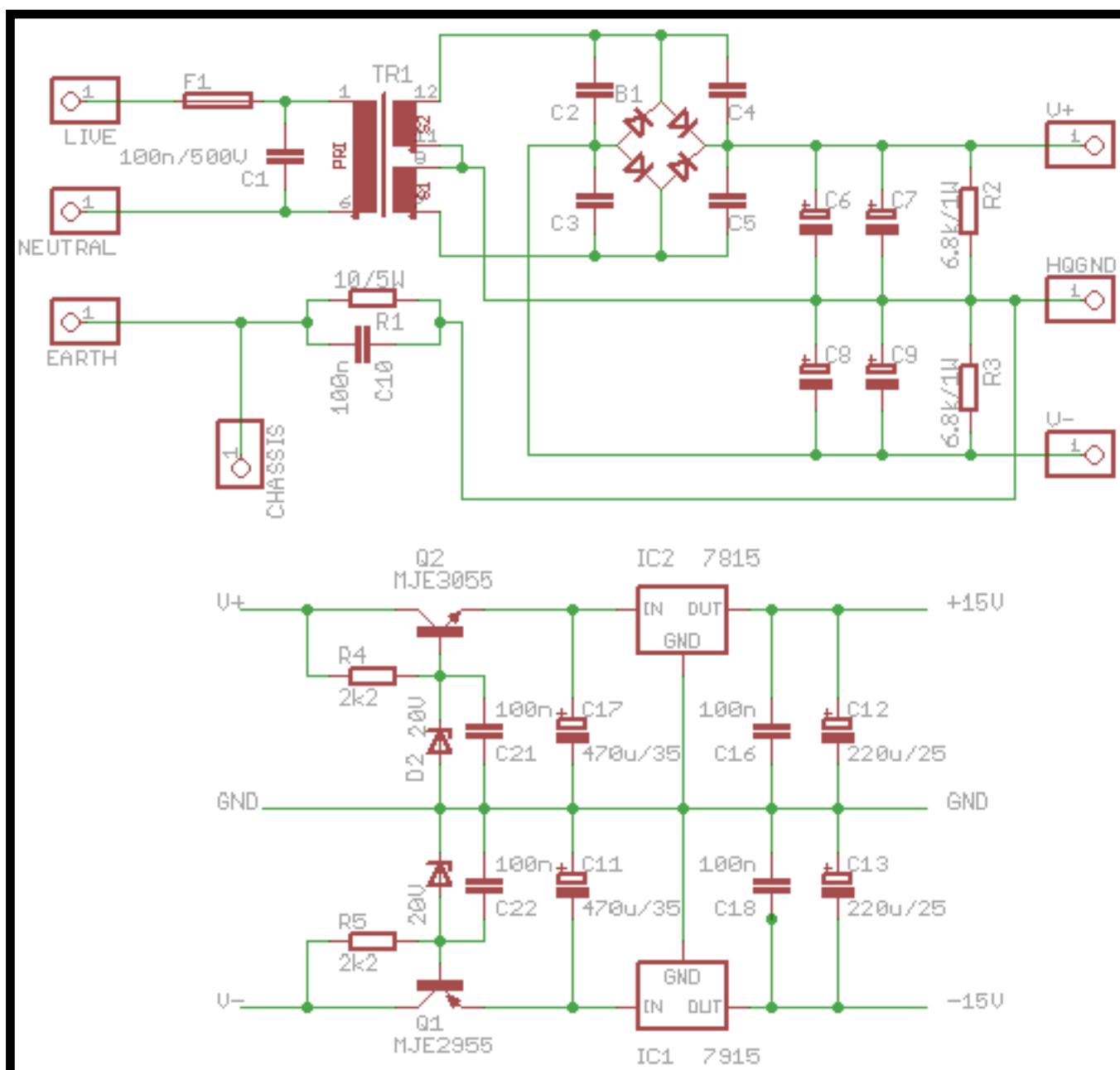

To achieve 100W in an 8 ohm load, 28.3Vrms or 40V peak is needed at the output. Due to the fact that a MOSFET output stage is used, about 48V rail voltage is needed to achieve this. Taking into account a 1V voltage drop in the rectifier, the needed transformer voltage is  $(48+1)/1.41 = 34.75\text{V}$ , so a dual 35V transformer would be about perfect. Most manufacturers of toroidal transformers specify their voltage rating under load, so the unloaded rail voltage will be some volts higher.

The rms current needed for 100W in 8 ohm would be  $28.3\text{Vrms}/8\text{ohm}=3.54\text{A rms}$ . Thus for a mono amplifier, the minimum transformer VA rating would become  $35*3.54=124\text{VA}$ . To give some extra current margin, a 150VA transformer would be great. If you intend to drive a 4 ohm load, this needs to be doubled. If you construct a stereo amplifier, this obviously needs to be doubled (again).

## Output relay configuration

The output relay is used to disconnect the speakers from the output of the amp and can be switched directly from the positive supply. A test with a 48V relay showed that it switches already at 27V, which allows a large supply range. The output relay can be used in different modes:

- Immediately from the pcb, by connecting V+ and GND from the board to the relay using two jumpers on the pinheader (connect 1+2 and 3+4). You might hear a thump when amp is switched on however.
- Using external protection circuitry, you can use the SPK pin for monitoring the output stage voltage.


An external protection circuit is strongly recommended and can be used for some or all of these functions:

- Delayed switch on
- Loss of AC detection
- DC protection
- Amplifier instability protection

A complete microcontroller based protection circuit with the above functions is now available, more information on the [PicProtection project page](#).


Below is a very simple circuit to prevent the thumb when the amplifier is switched on. It gives only a delayed switch on, so no DC protection. You can easily build it on vero board and connect it to the pinheader on the amp board. For convenience this RelayDelay circuit is now also available as [pcb](#) or [kit](#). Its working principle is very simple: when the amp is switched on, C1 is being charged through R2, therefore the voltage on the base of Q1 is slowly increasing and with it the voltage on the emitter of Q1, until the relay switches. With the current

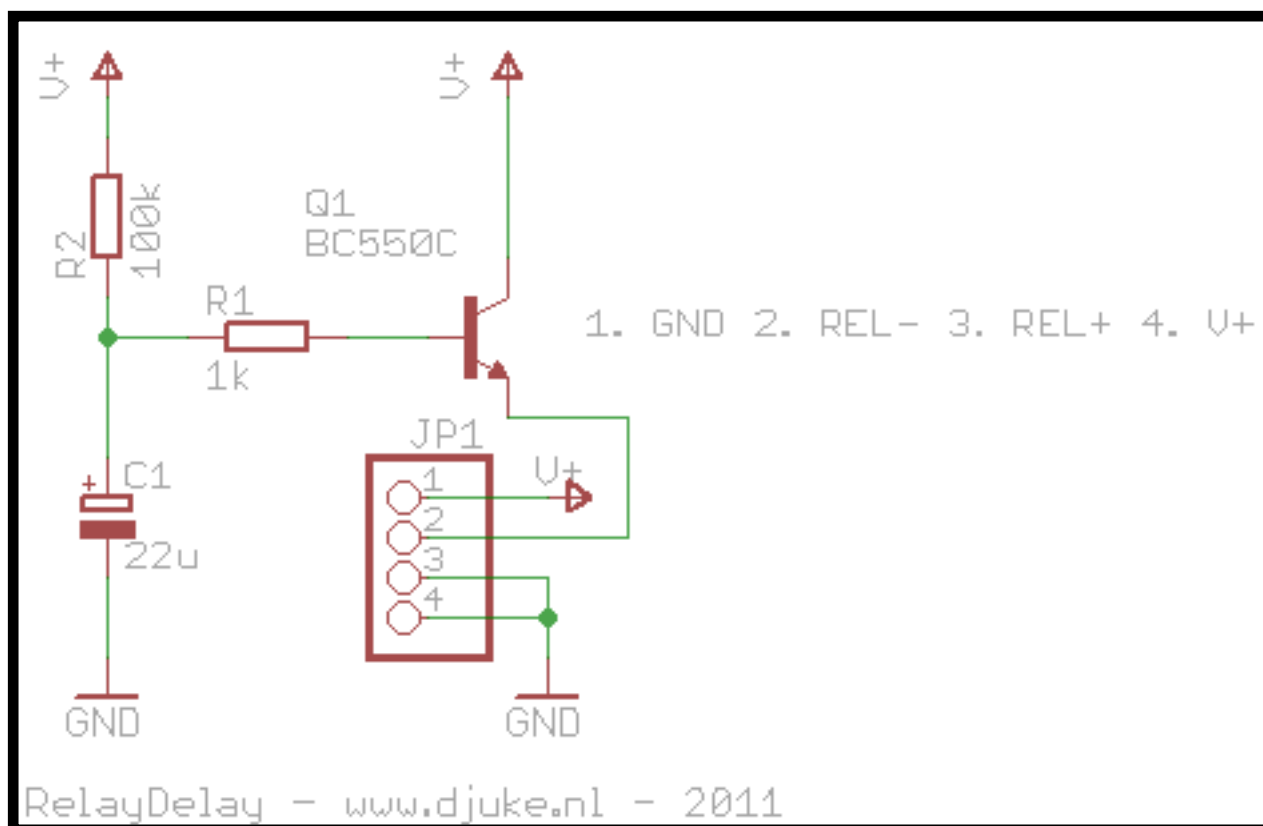
values of R2 and C1, it takes about 4s before the relay switches, but this can of course be easily changed.


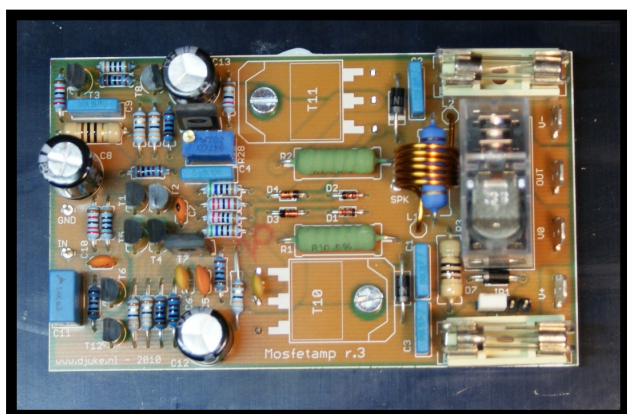
## PCB

The amplifier pcb is a single-layer board, using only through-hole components. All the components, including fuses, output inductor and output relay are placed on a board of only 6x10cm in size! The MOSFET's are located at the bottom of the board and the complete board can be attached to a heatsink using two bolts through the MOSFET's. Photos of the empty and assembled pcb are shown next.



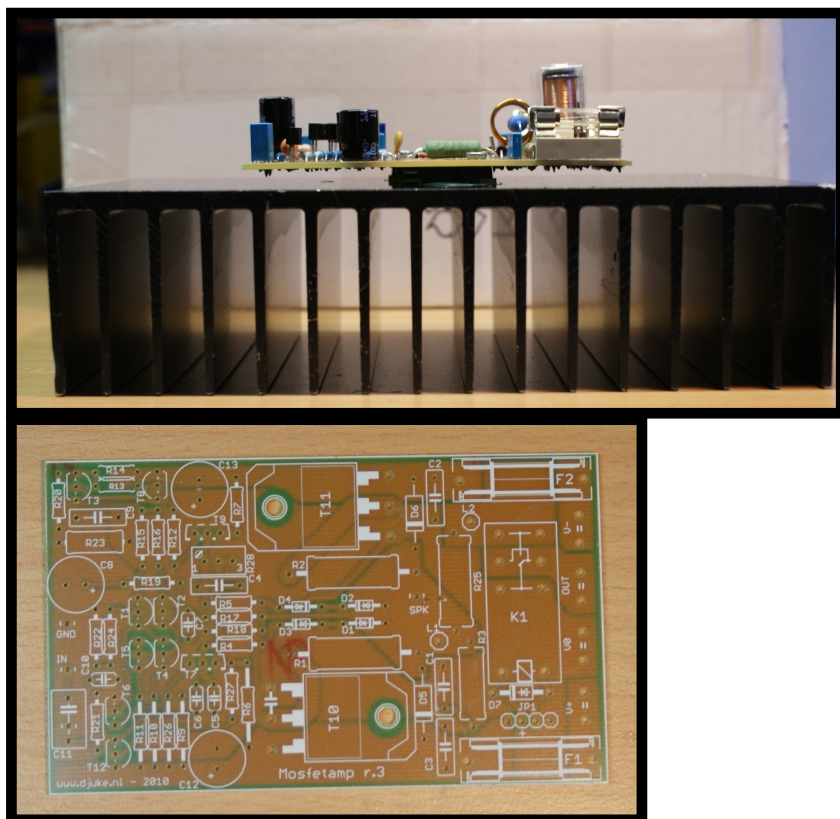


## Mounting layout

This mosfet power amplifier is very versatile, you can build several channels including filters or preamp in one cabinet. But maybe the most common use is a stereo power amplifier, for which the proposed mounting layout is shown in the next figure. To build it, the following components are needed:

- Cabinet (including heatsinks)
- Toroidal transformer
- 1x [Power entry with fuse](#)
- 1x Power switch
- 1x [Bridge rectifier](#)
- 1x [Supply kit \(pcb + components\)](#)
- 2x [Mosfet amp kit \(pcb + components\)](#)
- 1x [PicProtection kit for 2 channels \(main pcb, 2x detector pcb + components\)](#)


- [Connectors \(2x cinch, 2x speaker set\)](#)
- [Various wiring](#)

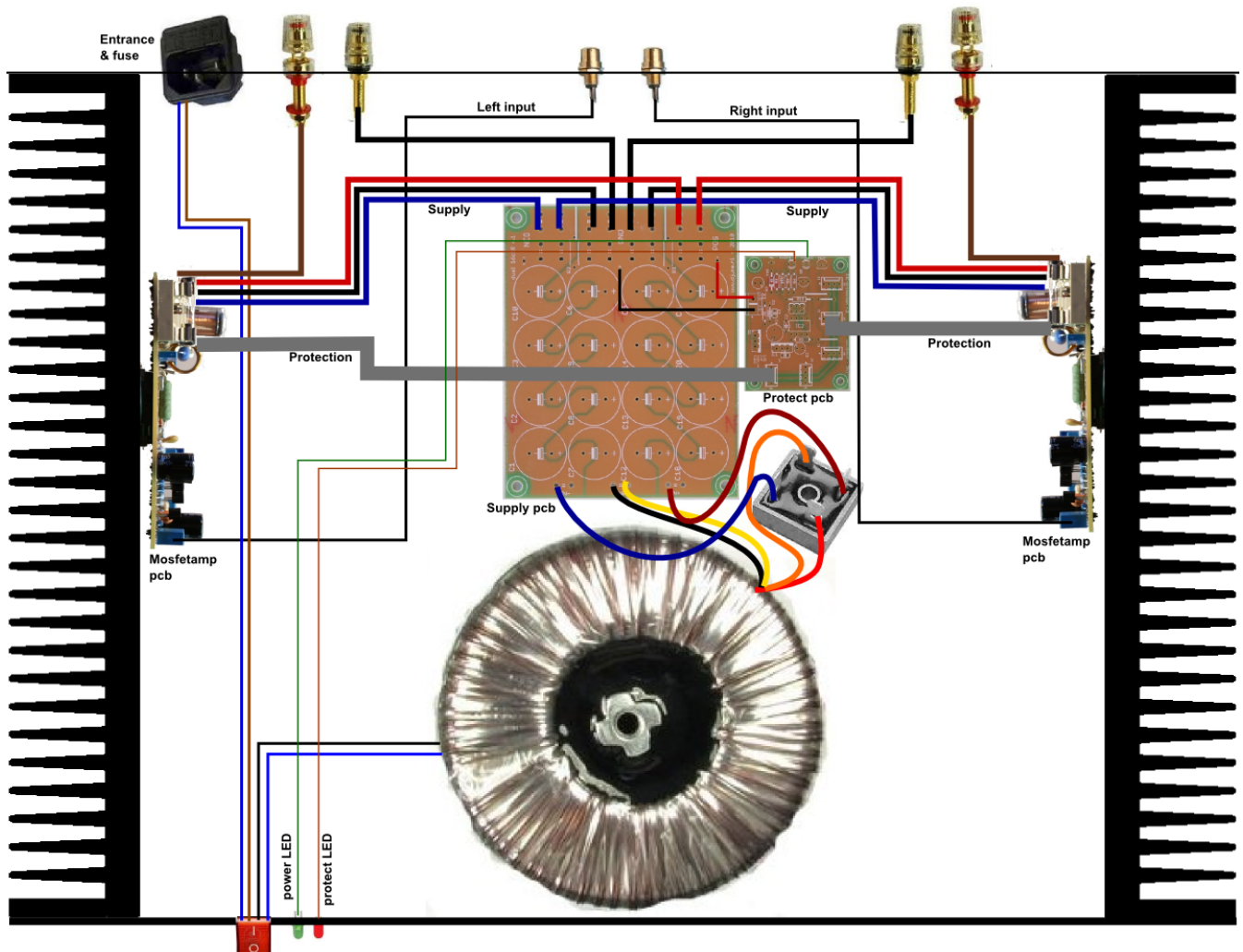A complete stereo version of this power amp can be built for between EUR 300,- and EUR 350,-


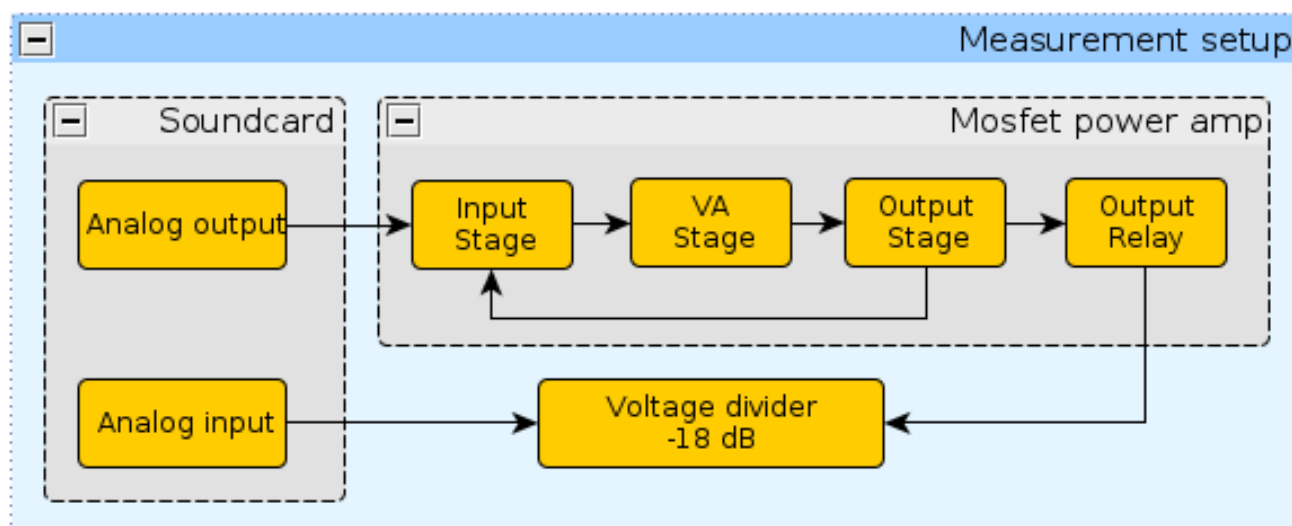
## Measurements

To measure the performance of my audio equipment I bought an E-mu 1212m sound card with outstanding performance. RMAA measurements of a loopback test with the card can be found [here](#). To measure the performance of the amplifier, I used the following measurement setup:



Because the output voltage of the mosfet amp is far too high to be connected directly to the analog input of the sound card, I used a simple voltage divider to attenuate this signal. This has some influence on the measurement results, especially the measured bandwidth, which seems lower, because the analog input of the sound card is not driven from a low impedance source anymore. THD and noise measurements are not influenced very much.

## Test conditions:

- Measurements at 24-bit, 96kHz.
- Analog output set to about -3 dB before amp starts clipping
- Supply: 2x30V 225VA toroidal transformer, 35A bridge rectifier, 2x13200uF capacitor bank gives 42V dual supply
- Test performed with single (mono) amplifier board
- Test performed without output load
- Test performed with 8 ohm resistive load connected to amplifier output

## Test results

Test results	DjukePoweramp NoLoad	DjukePoweramp 8oh
Frequency response (from 40 Hz to 15 kHz), dB:	+0.04, -0.23	+0.04, -0.24
Noise level, dB (A):	-102.5	-102.3
Dynamic range, dB (A):	102.4	102.4
THD (1kHz), %:	0.0004	0.0007
THD+Noise (1kHz) , % (A)	0.0016	0.0021
IMD + Noise, %:	0.0022	0.0028


Follow the link below for complete test results:



- [Overview.](#)
- [No load test.](#)
- [8 ohm test.](#)
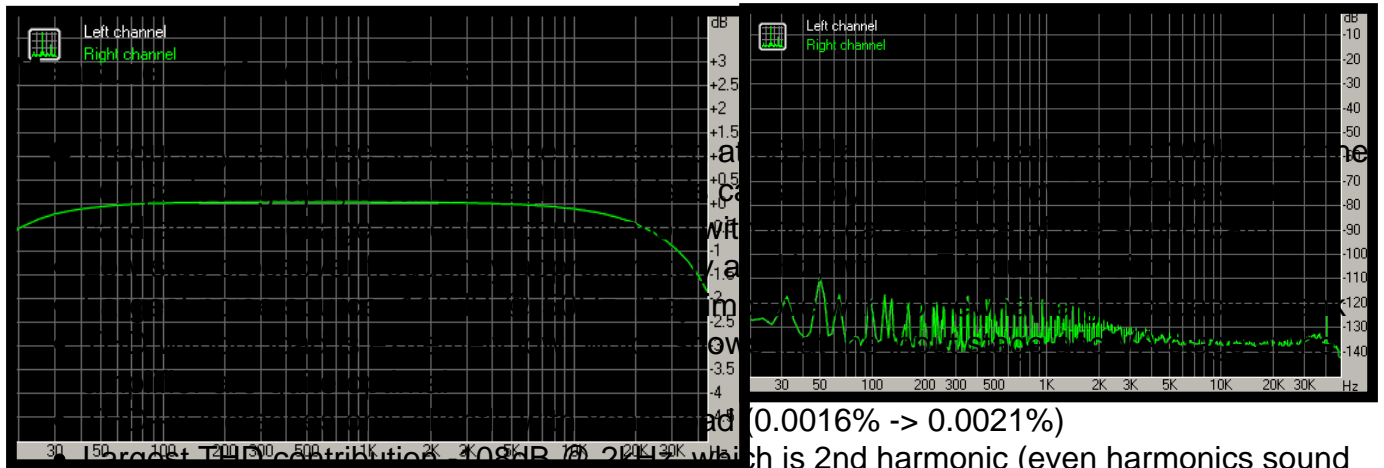
## Most interesting graphs

Frequency response, noise figure and total harmonic distortion measurements with 8 ohm load.



more pleasing than odd harmonics)


## General conclusions

The designed amplifier not only measures well, but also sounds great. Describing the sound of an amplifier is always a very subjective thing, but anyway there we go: it sounds very transparent and is full of detail. The low regions are very clear and direct (I believe because of the absence of passive components in the speaker) and the mid is very detailed (due to the active LR-crossover) and high is very smooth (due to the amplifiers two pole compensation, distortion stays low also above 1kHz). I believe that further increase in performance of this amplifier, can only be achieved by using a symmetric mirror-image, which makes it bigger, more complex and most likely less reliable.


## Update: Adding balanced inputs
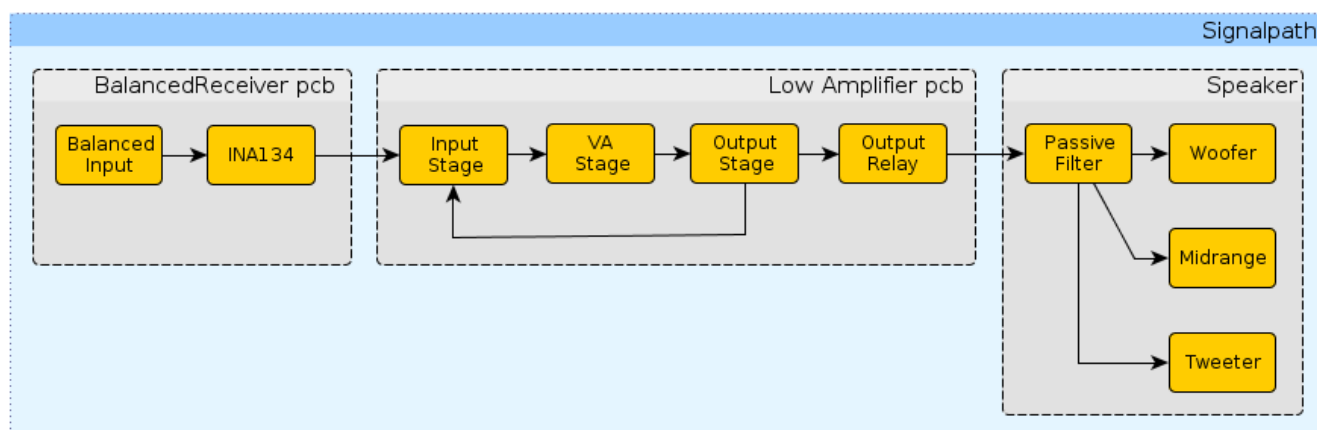
### BalancedReceiver design

A frequently asked question has been if it is possible to use balanced inputs in combination with the Mosfetamp. For this, I have designed a separate pcb based on the Burr Brown INA134 IC, that can be used easily in combination with the Mosfetamp as it has an integrated circuit that reduces the dual 50V power amp supply to dual 15V needed for the INA134. It is simply added in the signal path in front of the Mosfet amplifier like this:




The schematic is very straightforward. Considering the positive supply (negative part is similar), R4/C5 form a low pass filter that already considerably reduce the effect of the supply ripple (which can easily be a few Volts if the amplifier is near full output). Further supply reduction and smoothing is achieved with R2/D1 which gives a very stable 15V at the basis of Q1. The emitter of Q1 is about 0.7V lower at 14.3V. In combination with the large power supply reduction ratio of the INA134 this reduces the effect of power supply variations to the noise floor (as can be seen in the measurements below). As the current consumption of the INA134 is quite low, the power dissipation in Q1 remains low enough for a BC550 to be chosen. The INA134 connections are standard, with the balanced inputs on pin 2/3 and single-ended output on pin 6/1. Resistor R1 provides a choice of connecting supply GND to signal GND. Using a 0R resistor those can be fixed, but also different resistor values or even complete omission of R1 (based on the circuit after the BalancedReceiver) is an option.

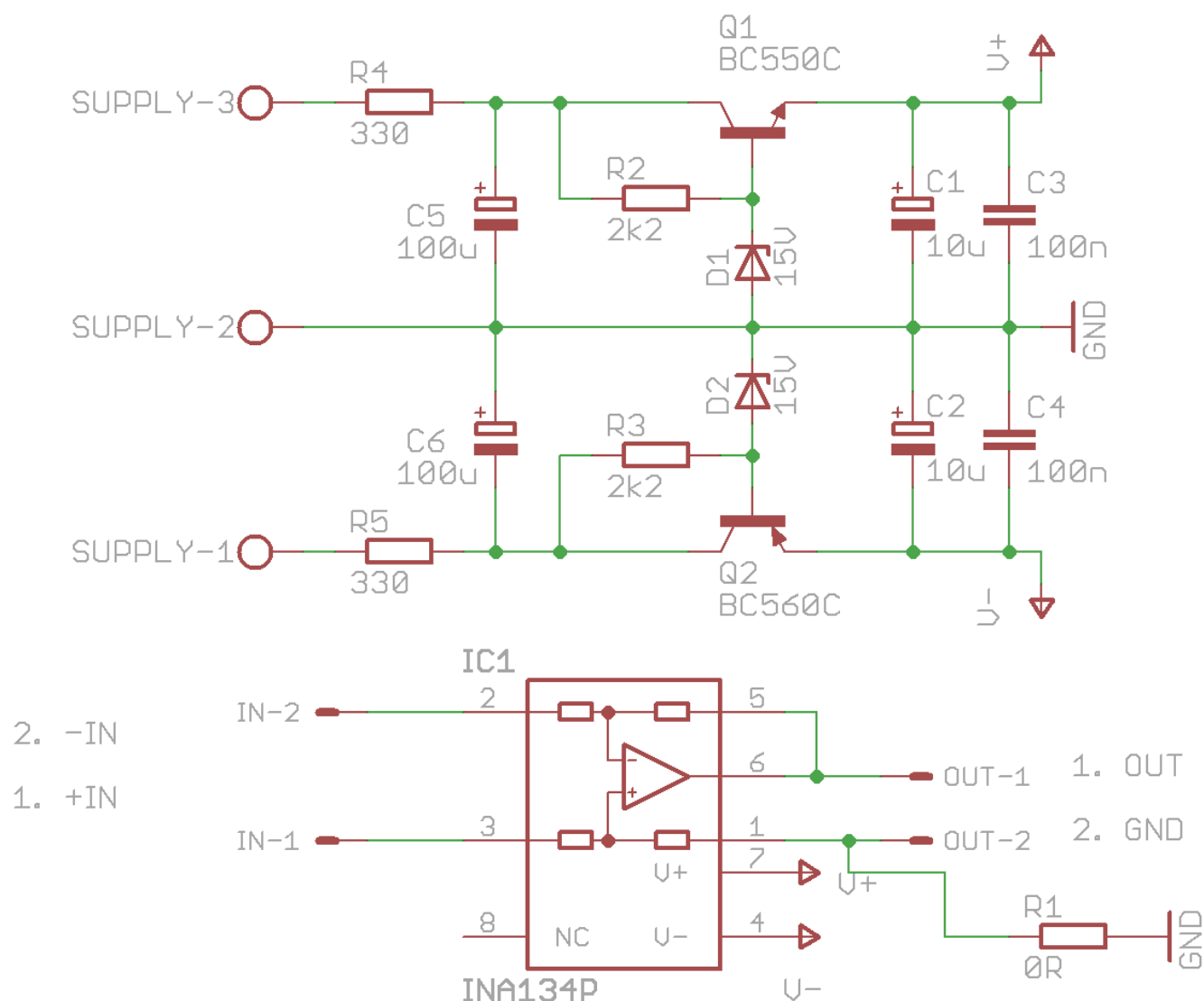

BalancedReceiver - [www.djuke.nl](http://www.djuke.nl) - 2015
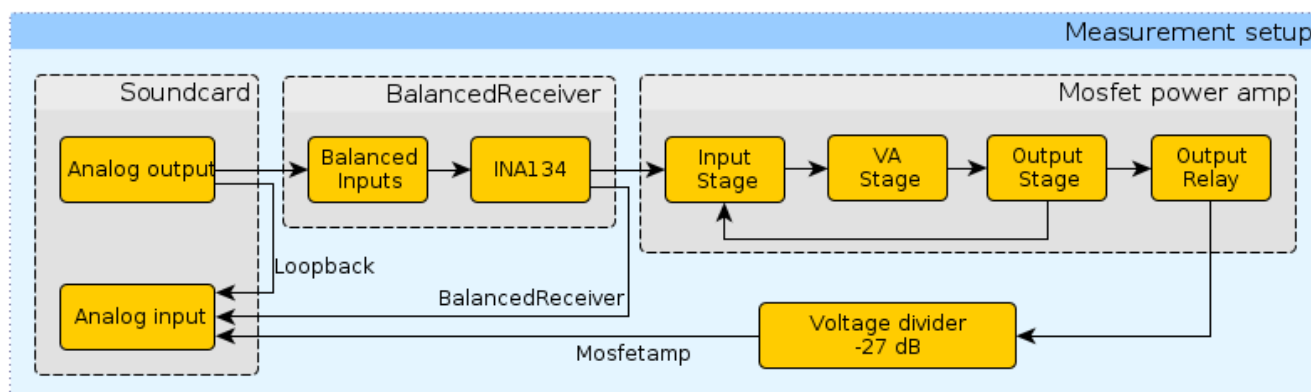
## BalancedReceiver measurements

To show how good the BalancedReceiver is, I did some RMAA measurements with my EMU-1212m sound card. The measurement setup is as follows:



At three positions in the chain, the results are measured:

- Reference Loopback measurement from soundcard Analog output directly to Analog input
- BalancedReceiver to show the individual contribution of the BalancedReceiver on distortion and noise
- BalancedReceiver + Mosfetamp


### Test conditions:

- Measurements at 24-bit, 96kHz.
- Analog output set to about -3 dB before amp starts clipping
- Supply: 2x30V 225VA torroidal transformer, 35A bridge rectifier, 2x13200uF capacitor bank gives 42V dual supply
- Mono mode (therefore ignore the crosstalk measurements below)
- Same sound card volume settings for all measurements

### Test results

Test	Loopback	BalancedReceiver	Mosfetamp No
Frequency response (from 40 Hz to 15 kHz), dB:	+0.02, -0.11	+0.01, -0.02	+0.03, -0.21
Noise level, dB (A):	-100.4	-99.2	-99.2
Dynamic range, dB (A):	100.5	99.2	99.1
THD, %:	0.0005	0.0005	0.0006
IMD + Noise, %:	0.0026	0.0030	0.0033

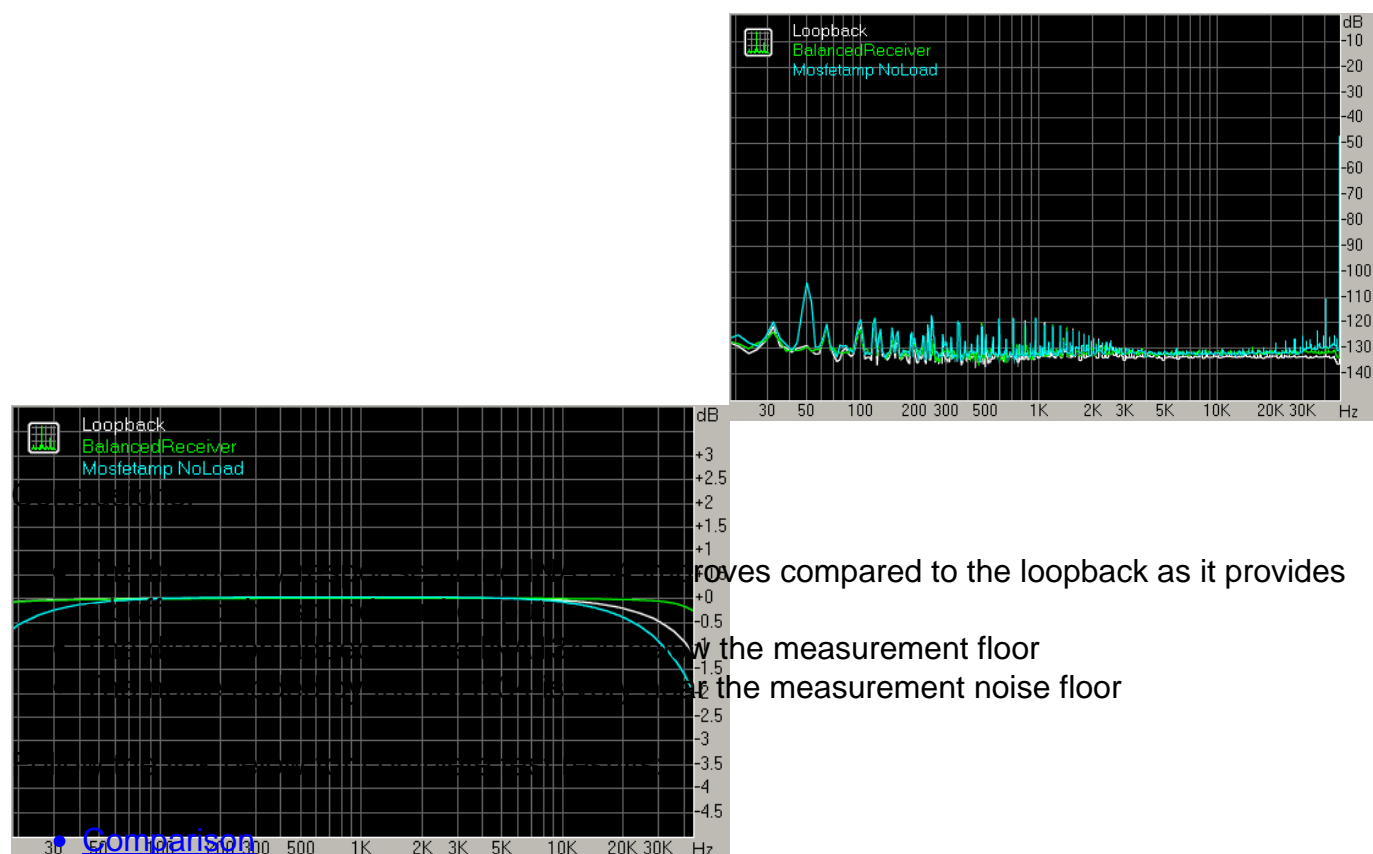Frequency response, noise figure and total harmonic distortion measurements comparison



#### • [Comparison](#)

- [Loopback](#)
- [BalancedReceiver](#)
- [BalancedReceiver + Mosfetamp](#)

## User gallery

This section contains images of users of the mosfet amplifier

---

### Tjerk



Two monoblocks, where the mosfet amplifier was modified to accomodate three (instead one one) mosfet output pairs.


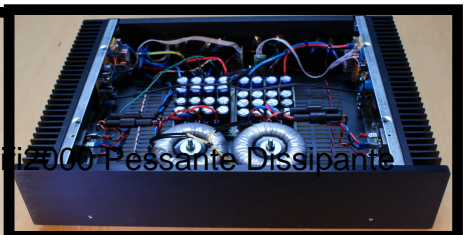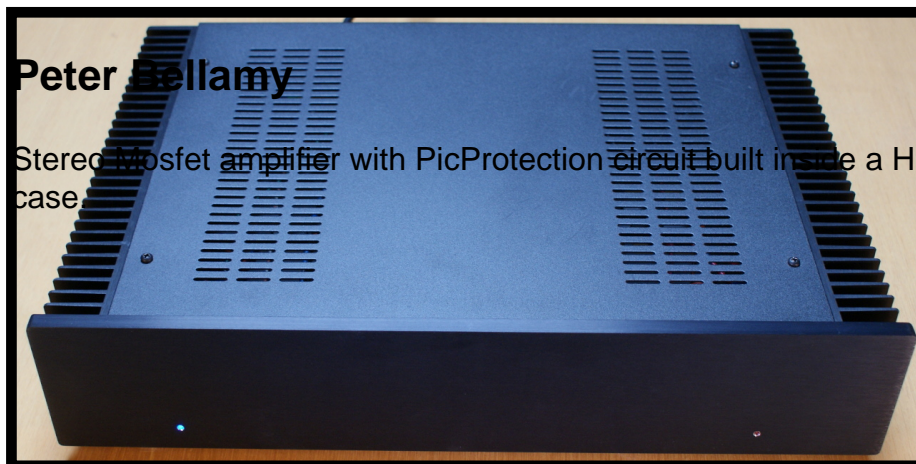
## Günter

Total of 6 mosfet amps combined with digital filters built inside 2 Hifi2000 cabinets






**Peter Bellamy**


Stereo Mosfet amplifier with PicProtection circuit built inside a Hifi2000 Pessante Dissipante case



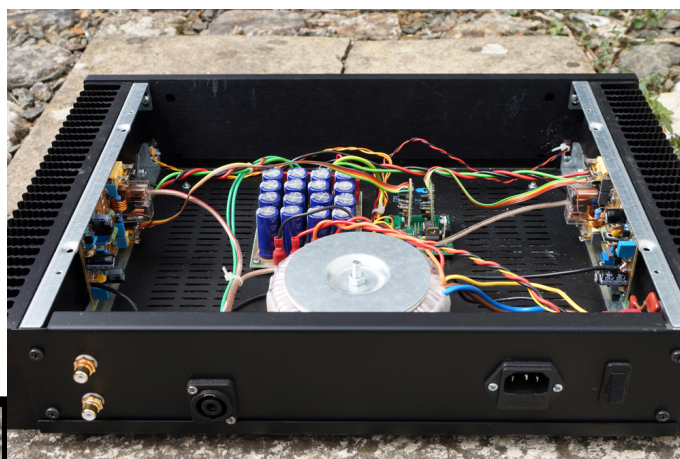**Arend van Oosten**

Stereo Mosfet amplifier used to drive a set of Martin Logan Aeries electrostates.



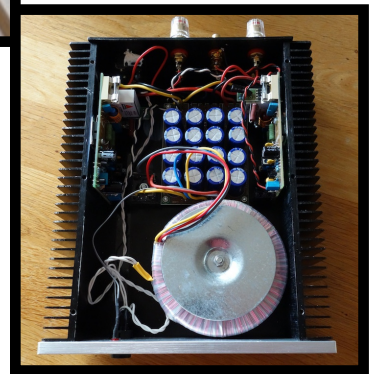

## Enrico Montani

The mosfet amplifier pcb is used as a replacement unit in a Sessionate bass amplifier.

