A user requested if it was possible to add balanced inputs to the Mosfet power amplifier. Based on that I made a small prototype using the Burr Brown INA134. Measurements show that this circuit adds hardly any noise and/or distortion. A section with the measurements was added to the Mosfet Power Amplifier project page.

Update: Kits are now available: BalancedReceiver kit